Two Semester System

Computer Department

First Year

Logic Project

Submitted to

Dr. Ihab Talkhan

By:	B.N	Sec	Taken Part
Doaa Magdy Ibrahim Muhammad	23	1	a
Rufaidah Muhammad Sayed Ahmed	25	1	a
Samaa Hazem Mohamed Abdel-latif	32	1	c
Abdelrahman Ashraf Mohamed Elsayed	35	1	b

2020-2021

#Input/Output

Inputs:

12 of Input Pins

Outputs:

3 of LEDs

3 of 7-Segment Display

#Number of gates used:

NOT Gate	113
AND Gate	293
OR Gate	185
NOR Gate	8
XOR Gate	88
Build-in Multiplexer	1
TOTAL without previous MUX	687
TOTAL	688